whatsapp: Fahad Hameed +92 323 509 4443, email: megalecture@gmail.com



WWW.MEGALECTURE.COM www.youtube.com/megalecture



1. George wishes to explore the rules for multiple capacitors. To do this, he constructs a circuit using three: C_1 is connected in series with C_2 ; these are both connected in parallel with C_3 . All are connected to a 6 V power supply. $C_1 = 10 \ \mu F, C_2 = 20 \ \mu F$ and $C_3 = 50 \ \mu F$.

Total for Question 1: 13

(a) Explain in terms of the flow of electrons how a potential difference is built up across a capacitor. [3]

- (b) Which of the following is correct? For two capacitors in series, irrespective of their capacitances, [1] the charge stored by the first will be...
 - i. Half of that stored by the second.
 - ii. The same as that stored by the second.
 - iii. Twice that stored by the second.
- (c) In any circuit, charge is conserved. Use this, in combination with Kirchoff's laws, to show that the total capacitance of two capacitors in series is given by $\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$. [3]





- (d) Using similar techniques, it can be shown that $C_{total} = C_1 + C_2$. For George's circuit, calculate the following:
 - i. The total capacitance of the circuit.

i. The reading on a voltmeter placed ecross-capacitor 1.



[3]





2.

Total for Question 2: 6

- (a) What is represented by the area underneath a graph of the potential difference across a resistor [1] against the charge stored by it?
- (b) From the equation $W = \frac{1}{2}QV$, derive two other equations for the energy stored in capacitor. One [3] should not include the term V and one should not include the term Q.

(c) State the effect of each of the following on the energy stored by a capacitor.i. Doubling the potential difference across it.

ii. Halving the capacitance.



whatsapp: Fahad Hameed +92 323 509 4443, email: megalecture@gmail.com



3. Ella charges a 50 μ F capacitor using a 6 V power supply. She then discharges it through a resistor of resistance R (connected in parallel).

Total for Question 3: 11

(a) Outline an experiment that Ella could perform to demonstrate the discharge characteristics of a [3] capacitor when it is discharging through a resistor. Include a circuit diagram.

(b) After 10 s, the charge has reduced by 39 μ C from its initial value of 300 μ C. Calculate *R*.

[2]



Page 5 of 7



(c) Calculate the current in the circuit 2τ after the switch has been turned on.

[2]

(d) Once it has completely discharged, Ella recharges the capacitor using the same 6 V power supply. [2] Calculate the potential difference across the capacitor after 5 s.





(e) Sketch, on a single set of axes, the variation of V_c , V_R and V_0 with time during charging. V_C , V_R and V_0 are the potential differences across the capacitor, the resistor and the power supply respectively. [2]

www.megalecture.com



Page 7 of 7