

**AQA, Edexcel**

**A Level**

# A Level Physics

ELECTRICAL CIRCUITS:

Complete Circuits 1

Name:



Mathsmadeeasy.co.uk

Total Marks: /30



1.

Total for Question 1: 8

(a) Define electrical work,  $W$ , in terms of potential difference,  $V$ , and charge,  $Q$ . Using this relationship, show that  $P = I^2R$  [2]

(b) The P.D. across a  $5.0 \Omega$  resistor is measured as  $6.0 \text{ V}$ . What power is it dissipating? [2]

(c) An LED is connected in series with an ammeter and a power supply. A voltmeter is connected across the LED. They read  $2.2 \text{ A}$  and  $4.6 \text{ V}$ . If it is left on for 1 hour and 15 minutes, how much work is done by the LED? [2]

- (d) Sketch how the electrical work done by the resistor at a given point in time would vary with the resistance of the resistor. Assume the P.D. across the resistor is constant. [2]

[www.megalecture.com](http://www.megalecture.com)

2. This question exploits Kirchoff's laws to determine the resistances of several components in Figure 1.

Total for Question 2: 10

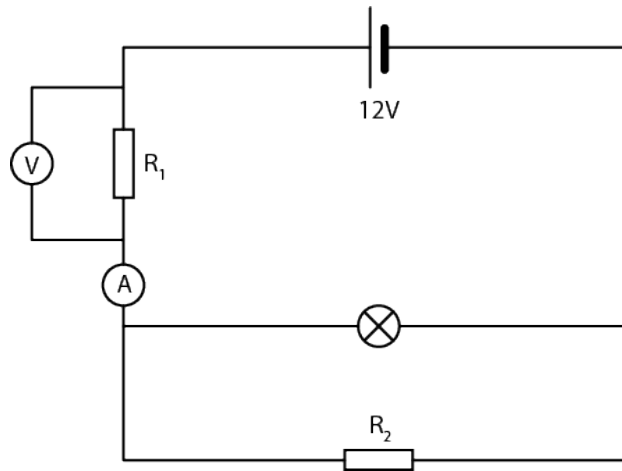


Figure 1: A circuit containing two resistors, a voltmeter, an ammeter, a cell and a bulb.

Tom notes that the the bulb has an effective resistance of  $5.0 \Omega$ , that the voltmeter reads  $2.0 \text{ V}$  and that the ammeter reads  $3.5 \text{ A}$ .

(a) State Kirchoff's First Circuit Law. What implications does it have for the charge entering and leaving a circuit junction? [2]

(b) State Kirchoff's Second Circuit Law. [1]

(c) Calculate  $R_1$ . [1]

(d) Calculate  $R_2$ . [3]

(e) Calculate the power dissipated by the bulb. [1]

(f) The bulb dissipates 75% of its power as heat and converts the rest to light. What is the efficiency of this circuit as a means of lighting? [2]

[www.megalecture.com](http://www.megalecture.com)



3. Based on the conservation of charge and of energy, it is possible to derive several laws that dictate how the total effective resistance in a circuit varies when a combination of resistors are used in series and/or parallel.

Total for Question 3: 8

- (a) Use Kirchoff's and Ohm's laws to derive an expression for the total effective resistance of two resistors,  $R_{1-2}$ , in series. [2]

- (b) Using a similar technique, show that for two resistors in parallel,  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ . [3]

- (c) Two resistors ( $1.0 \Omega$  and  $2.0 \Omega$ ) connected in parallel are linked in series to a  $3.0 \Omega$  resistor. All of this is in parallel with a fourth resistor. If the total effective resistance is  $1.0 \Omega$ , what is the resistance of the fourth resistor? [3]

4. Most thermistors and LDRs rely on the properties of semiconductors to vary their resistance.

Total for Question 4: 4

(a) Briefly explain how changes in temperature cause a change in the resistance of a thermistor. For an ntc thermistor. will the resistance increase or decrease as temperature rises? [2]

(b) Outline the mechanism behind an LDR's variable resistance. [2]

[www.megalecture.com](http://www.megalecture.com)