



## Q1

- 5 (a) (i) resistance =  $V/I$  ..... C1  
 $= 6.0/(40 \times 10^{-3})$   
 $= 150 \Omega$  ..... A1  
 (no marks for use of gradient)
- (ii) at 8.0 V, resistance =  $8.0/(50 \times 10^{-3}) = 160 \Omega$  ..... C1  
 change =  $10 \Omega$  ..... A1 [4]
- (b) (i) straight line through origin ..... M1  
 passes through  $I = 40 \text{ mA}$ ,  $V = 8.0\text{V}$  ..... A1
- (ii) current in both must be 40 mA ..... C1  
 e.m.f. =  $8.0 + 6.0 = 14.0 \text{ V}$  ..... A1 [4]

## Q2.

- 7 (a) (i)  $P = VI$   
 current =  $60/240 = 0.25 \text{ A}$   
 (ii)  $R (= VI) = 240/0.25$   
 $= 960 \Omega$  C1  
 A1  
 M1  
 A0 [3]
- (b)  $R = \rho L/A$  (wrong formula, 0/3)  
 $960 = (7.9 \times 10^{-7} \times L)/(\pi \times \{6.0 \times 10^{-6}\}^2)$   
 $L = 0.137 \text{ m}$  C1  
 (use of  $A = 2\pi r$ , then allow 1/3 marks only for resistivity formula) C1  
 A1 [3]
- (c) e.g. the filament must be coiled/it is long for a lamp  
 (allow any sensible comment based on candidate's answer for  $L$ ) B1 [1]

Total [7]

## Q3.

- 8 (a)  $V/E = R/R_{\text{tot}}$  or  $0.5 = I \times 3900$  C1  
 $1.0/1.5 = R/(R + 3900)$  or  $1.0 = 0.5R/3900$  M1  
 $R = 7800\Omega$ . or  $R = 7800\Omega$  A0 [2]
- (b)  $V = 1.5 \times (7800/(7800 + 1250))$  or  $I = 1.5/(7800 + 1250)$  C1  
 $= 1.29 \text{ V}$  or  $V = IR = 1.29 \text{ V}$  A1 [2]
- (c) Combined resistance of R and voltmeter is  $3900 \Omega$   
 reading at  $0^\circ\text{C}$  is  $0.75 \text{ V}$  C1  
 A1 [2]

Total [6]

## Q4.


**MEGA LECTURE**

<b>6</b>	(a) (i) lines normal to plate and equal spacing (at least 4 lines) direction from (+) to earthed plate	B1 B1	[2]
	(ii) $E = 160/0.08$ $= 2.0 \times 10^3 \text{ V m}^{-1}$	M1 A0	[1]
	(b) (i) correct directions with line of action of arrows passing through charges	B1	[1]
	(ii) force $= Eq$ $= 2.0 \times 10^3 \times 1.2 \times 10^{-15}$ $= 2.4 \times 10^{-12} \text{ N}$	C1 A1	[2]
	(iii) couple = force $\times$ perpendicular separation $= 2.4 \times 10^{-12} \times 2.5 \times 10^{-3} \times \sin 35^\circ$ $= 3.4(4) \times 10^{-15} \text{ N m}$	M1 A1	[2]
	(iv) either rotates to align with the field or oscillates (about a position) with the positive charge nearer to the earthed plate/clockwise	M1 A1	[2]

Q5.

<b>7</b>	(a) potential difference/current	B1	[1]
	(b) (i) 1) 1.13 W 2) 1.50 V	B1	[1]
	(ii) power $= V^2 / R$ or power $= VI$ and $V = IR$ $R = 1.50^2/1.13$ $= 1.99 \Omega$	C1 A1	[2]
	(iii) either $E = IR + Ir$ or $I = 1.5 / 2.0 (= 0.75 \text{ A})$ $3.0 = 1.5 + 0.75r$ $r = 2.0 \Omega$ voltage divided between $R$ and $r$ p.d. across $R$ = p.d. Across $r = 1.5$	C1 C1	
		so $R = r = 1.99 \Omega$	A1 [3]
	(c) larger p.d. across $R$ means smaller p.d. across $r$ smaller power dissipation at larger value of $V$ since power is $VI$ and $I$ is same for $R$ and $r$	M1 A1 A1	[3]

Q6.



7	(a) lamp C lamp is shorted	M1 A1	[2]
	(b) shorted lamp A would cause damage to the supply/lamps /blow fuse in supply	B1	[1]
	(c) $15 \Omega$	B1	[1]
	(d) (i) $V = IR$ $R = 30 \Omega$	C1 A1	[2]
	(ii) $P = VI$ or $P^2 R$ or $V^2 / R$ $P = 1.2 \text{ W}$	C1 A1	[2]
	(e) filament is cold when measuring with ohm-meter in (b) resistance of filament rises as temperature rises	B1 B1	[2]

Q7.

2	(a) force <u>per unit positive charge</u> (on a small test charge)	B1	[1]
	(b) field strength = $(210 / \{1.5 \times 10^{-2}\}) = 1.4 \times 10^4 \text{ N C}^{-1}$	A1	[1]
	(c) (i) acceleration = $Eq / m$ $= (1.4 \times 10^4 \times 1.6 \times 10^{-19}) / (9.1 \times 10^{-31})$ $= 2.5 \times 10^{15} \text{ m s}^{-2}$ ( $2.46 \times 10^{15}$ ) towards positive plate / upwards (and normal to plate)	C1 C1 A1 B1	[4]
	(ii) time = $2.4 \times 10^{-9} \text{ s}$	A1	[1]
	(d) either vertical displacement after acceleration for $2.4 \times 10^{-9} \text{ s}$ $= \frac{1}{2} \times 2.46 \times 10^{15} \times (2.4 \times 10^{-9})^2$ $= 7.1 \times 10^{-3} \text{ m}$ ( $0.71 \text{ cm} < 0.75 \text{ cm}$ and) so will pass between plates i.e. valid conclusion based on a numerical value	C1 A1 A1	[3]
	or $0.75 \times 10^{-2} = \frac{1}{2} \times 2.46 \times 10^{15} \times t^2$ t is time to travel 'half-way across' plates = $2.47 \times 10^{-9} \text{ s}$ ( $2.4 \text{ ns} < 2.47 \text{ ns}$ ) so will pass between plates i.e. valid conclusion based on a numerical value	(C1) (A1) (A1)	

Q8.



<b>6 (a) (i)</b>	1 total resistance = $0.16 \Omega$	A1	
2 e.m.f. = either $(14 - E)$ or $(E - 14)$		A1	[2]
<b>(ii)</b> either $14 - E = 42 \times 0.16$ or $(E - 14) = -42 \times 0.16$		C1	
$E = 7.3 \text{ V}$		A1	[2]
<b>(b) (i)</b> charge = $It$ = $12.5 \times 4 \times 60 \times 60$ = $1.8 \times 10^5 \text{ C}$		C1	
<b>(ii)</b> either energy = $EQ$ or energy = $EIt$ either energy = $14 \times 1.8 \times 10^5$ or energy = $14 \times 12.5 \times 4 \times 3600$ = $2.52 \times 10^6 \text{ J}$		C1	
<b>(iii)</b> energy = $I^2Rt$ or $VIt$ and $V = IR$ = $12.5^2 \times 0.16 \times 4 \times 3600$ = $3.6 \times 10^5 \text{ J}$		C1	
<b>(c)</b> efficiency = $(2.52 \times 10^6 - 3.6 \times 10^5) / (2.52 \times 10^6)$ = 86%		C1	
		A1	[2]

**Q9.**

<b>6 (a)</b> either $P = VI$ and $V = IR$ or $P = V^2 / R$	C1	
resistance = $38.4 \Omega$	A1	[2]
<b>(b)</b> zero	B1	
1.5 kW	B1	
3.0 kW	B1	
0.75 kW	B1	
2.25 kW	B1	[5]

**Q10.**



<b>6 (a) (i)</b>	$E = V/d$ ..... = $350 / (2.5 \times 10^{-2})$ ..... = $1.4 \times 10^4 \text{ N C}^{-1}$ .....	C1	
<b>(ii)</b>	$\text{force} = Eq$ ..... = $1.4 \times 10^4 \times 1.6 \times 10^{-19}$ ..... = $2.24 \times 10^{-15}$ .....	C1 M1 A0	[2]
<b>(b) (i)</b>	$F = ma$ ..... $a = (2.24 \times 10^{-15}) / (9.1 \times 10^{-31})$ ..... = $2.46 \times 10^{15} \text{ m s}^{-2}$ ... (allow $2.5 \times 10^5$ ) .....	C1 A1	[2]
<b>(ii)</b>	$s = \frac{1}{2}at^2$ ..... $2.5 \times 10^{-2} = \frac{1}{2} \times 2.46 \times 10^{15} \times t^2$ ..... $t = 4.5 \times 10^{-9} \text{ s}$ .....	C1 A1	[2]
<b>(c)</b>	either gravitational force is normal to electric force or electric force horizontal, gravitational force vertical ..... special case: force/acceleration due to electric field >> force/acceleration due to gravitational field, allow 1 mark	B2	[2]

**Q11.**

<b>7 (a) (i)</b>	$R$ .....	B1	[1]
<b>(ii)</b>	$0.5R$ .....	B1	[1]
<b>(iii)</b>	$2.5R$ ... (allow e.c.f. from (ii)) .....	B1	[1]
<b>(b) (i)</b>	$I_1 + I_2 = I_3$ .....	B1	[1]
<b>(ii)</b>	$E_2 = I_3 R + I_2 R$ .....	B1	[1]
<b>(iii)</b>	$E_1 - E_2 = 2I_1 R - I_2 R$ .....	B1	[1]

**Q12.**

<b>7 (a)</b>	$\infty$ ..... $2R$ .....	A1	
	$R$ .....	A1	[3]
<b>(b) (i)</b>	$I_1 + I_3 = I_2 + I_4$ .....	A1	[1]
<b>(ii)</b>	$E_2 - E_1 = I_3 R$ .....	A1	[1]
<b>(iii)</b>	$E_2 = I_3 R + 2I_4 R$ .....	A1	[1]

**Q13.**



- 5 (a) region/area where a charge experiences a force ..... B1 [1]
- (b) (i) left-hand sphere (+), right-hand sphere (-) ..... B1 [1]
- (ii) 1 correct region labelled C within 10 mm of central part of plate otherwise within 5 mm of plate ..... B1 [1]
- 2 correct region labelled D area of field not included for (b)(ii)1 ..... B1 [1]
- (c) (i) arrows through P and N in correct directions ..... B1 [1]
- (ii) torque = force  $\times$  perpendicular distance (between forces) ..... C1  
 $= 1.6 \times 10^{-19} \times 5.0 \times 10^4 \times 2.8 \times 10^{-10} \times \sin 30$   
 $= 1.1 \times 10^{-24}$  N m ..... A1 [2]

Q14.

- 6 (a) (i)  $P = VI$  ..... C1  
 $60 = 12 \times I$   
 $I = 5.0$  A ..... A1 [2]
- (ii) either  $V = IR$  or  $P = I^2R$  or  $P = V^2/R$  ..... C1  
either  $12 = 5 \times R$  or  $60 = 5^2 \times R$  or  $60 = 12^2/R$  ..... M1  
 $R = 2.4 \Omega$  ..... A0 [2]
- (b)  $R = \rho L/A$  ..... C1  
 $A = \pi \times (0.4 \times 10^{-3})^2 (= 5.03 \times 10^{-7})$  ..... C1  
 $L = (2.4 \times 5.03 \times 10^{-7})/(1.0 \times 10^{-6})$   
 $= 1.2$  m ..... A1 [3]
- (c) resistance is halved ..... M1  
either current is doubled or power  $\propto 1/R$  ..... M1  
power is doubled ..... A1 [3]

Q15.


**MEGA LECTURE**

- 6 (a) either  $P \propto V^2$  or  $P = V^2/R$  ..... C1  
 reduction =  $(230^2 - 220^2)/230^2$   
 = 8.5 % ..... A1 [2]
- (b) (i) zero ..... A1 [1]  
 (ii) 0.3(0)A ..... A1 [1]
- (c) (i) correct plots to within  $\pm 1$  mm ..... B1 [1]  
 (ii) reasonable line/curve through points giving current as 0.12A  
 allow  $\pm 0.005A$  ..... B1 [1]  
 (iii)  $V = IR$  ..... C1  
 $V = 0.12 \times 5.0$   
 = 0.6(0)V ..... A1 [2]
- (d) circuit acts as a potential divider/current divides/current in AC not the same as  
 current in BC ..... B1  
 resistance between A and C not equal to resistance between C and B ..... B1  
 or current in wire AC  $\times R$  is not equal to current in wire BC  $\times R$  ..... B1 [2]  
 any 2 statements

**Q16.**

- 6 (a) (i) movement/flow of charged particles ..... B1 [1]  
 (ii) work done per unit charge (transferred) ..... B1 [1]
- (b) straight line through origin  
 resistance =  $V/I$ , with values for  $V$  and  $I$  shown  
 =  $20\Omega$   
 (using the gradient loses the last mark) ..... B1  
 M1  
 A0 [2]
- (c) (i) 0.5A ..... A1 [1]  
 (ii) either resistance of each resistor is  $20\Omega$  or total current = 0.8A  
 either combined resistance =  $10\Omega$  or  $R = E/I = 10\Omega$  ..... C1  
 A1 [2]
- (d) (i) 10V ..... A1 [1]  
 (ii) power =  $EI$   
 =  $10 \times 0.2 = 2.0W$  ..... C1  
 A1 [2]

**Q17.**



5 (a) (i) $I = 12 / (6 + 12)$ minimum current = 0.67 A	C1 A1 [2]
(ii) correct start and finish points correct shape for curve with decreasing gradient	M1 A1 [2]
(b) maximum current = 2.0 A minimum current = 0	A1 A1 [2]
(c) (i) smooth curve starting at (0,0) with decreasing gradient end section not horizontal	M1 A1 [2]
(ii) full range of current / p.d. possible or currents / p.d. down to zero or brightness ranging from off to full brightness	B1 [1]

## Q18.

5 (a) (i) energy converted from chemical to electrical when charge flows through cell or round <u>complete</u> circuit	B1
(ii) (resistance of the cell) causing loss of voltage or energy loss in cell	B1 [2]
(b) (i) $E_B - E_A = I(R + r_B + r_A)$ $12 - 3 = I(3.3 + 0.1 + 0.2)$ $I = 2.5 \text{ A}$	C1 A1 [2]
(ii) Power = $E \times I$ = $12 \times 2.5$ = 30 W	C1 A1 [2]
(iii) $P = I^2 \times R$ = $(2.5)^2 \times 3$ = $22.5 \text{ Js}^{-1}$ or $P = V^2 / R$ = $9^2 / 3.6$ or $P = VI$ = 9 × 2.5	C1 A1 [2]
(c) power supplied from cell B is greater than energy lost per second in circuit	B1 [1]

## Q19.

5 (a) (i) Start from (0,0) and smooth curve in correct direction Curve correct for end section never horizontal	B1 B1 [2]
(ii) $R = V / I$ hence take co-ords of $V$ and $I$ from graph and calculate $V / I$	B1 [1]
(b) (i) each lamp in parallel has a greater p.d. / greater current lamp hotter resistance of lamps in parallel greater	M1 M1 A1 [3]
(ii) $P = V^2 / R$ or $P = VI$ and $V = IR$ $R = 144 / 50 = 2.88$ for each lamp total $R = 1.44 \Omega$	C1 C1 A1 [3]



## Q20.

- 4 (a) (i)  $R = V^2 / P$  or  $P = IV$  and  $V = IR$   
 $= (220)^2 / 2500$   
 $= 19.4\Omega$  (allow 2 s.f.) C1  
A1 [2]
- (ii)  $R = \rho l / A$   
 $l = [19.4 \times 2.0 \times 10^{-7}] / 1.1 \times 10^{-6}$   
 $= 3.53\text{m}$  (allow 2 s.f.) C1  
C1  
A1 [3]
- (b) (i)  $P = 625, 620$  or  $630\text{W}$  A1 [1]
- (ii)  $R$  needs to be reduced  
*Either* length  $\frac{1}{4}$  of original length  
or area  $4\times$  greater  
or diameter  $2\times$  greater A1 [2]

## Q21.

- 5 (a) (i) sum of e.m.f.'s = sum of p.d.'s around a loop/circuit B1 [1]
- (ii) energy B1 [1]
- (b) (i)  $2.0 = I \times (4.0 + 2.5 + 0.5)$   
 $I = 0.286\text{A}$  (allow 2 s.f.)  
(*If total resistance is not  $7\Omega$ , 0/2 marks*) C1  
A1 [2]
- (ii)  $R = [0.90 / 1.0] \times 4 (= 3.6)$   
 $V = I R = 0.286 \times 3.6 = 1.03\text{V}$   
(*If factor of 0.9 not used, then 0/2 marks*) C1  
A1 [2]
- (iii)  $E = 1.03\text{V}$  A1 [1]
- (iv) either no current through cell B  
or p.d. across  $r$  is zero B1 [1]

## Q22.

- 4 (a) total resistance =  $20\text{ (k}\Omega)$  C1  
current =  $12 / 20\text{ (mA)}$  or potential divider formula C1  
p.d. =  $[12 / 20] \times 12 = 7.2\text{V}$  A1 [3]
- (b) parallel resistance =  $3\text{ (k}\Omega)$  C1  
total resistance  $8 + 3 = 11\text{ (k}\Omega)$  C1  
current =  $12 / 11 \times 10^3 = 1.09 \times 10^{-3}$  or  $1.1 \times 10^{-3}\text{A}$  A1 [3]
- (c) (i) LDR resistance decreases  
total resistance (of circuit) is less hence current increases M1  
A1 [2]
- (ii) resistance across XY is less  
less proportion of  $12\text{V}$  across XY hence p.d. is less M1  
A1 [2]

## Q23.

- 4 (a)** electric field strength is the force per unit positive charge (acting on a stationary charge) B1 [1]
- (b) (i)**  $E = V/d$  C1  
 $= 1200 / 14 \times 10^{-3}$   
 $= 8.57 \times 10^4 \text{Vm}^{-1}$  A1 [2]
- (ii)**  $W = QV$  or  $W = F \times d$  and therefore  $W = E \times Q \times d$  C1  
 $= 3.2 \times 10^{-19} \times 1200$   
 $= 3.84 \times 10^{-16} \text{J}$  A1 [2]
- (iii)**  $\Delta U = mgh$  C1  
 $= 6.6 \times 10^{-27} \times 9.8 \times 14 \times 10^{-3}$   
 $= 9.06 \times 10^{-28} \text{J}$  A1 [2]
- (iv)**  $\Delta K = 3.84 \times 10^{-16} - \Delta U$  A1 [1]  
 $= 3.84 \times 10^{-16} \text{J}$
- (v)**  $K = \frac{1}{2}mv^2$  C1  
 $v = [(2 \times 3.8 \times 10^{-16}) / 6.6 \times 10^{-27}]^{1/2}$   
 $= 3.4 \times 10^5 \text{ms}^{-1}$  A1 [2]

**Q24.**

- 5 (a) (i)** sum of currents into a junction = sum of currents out of junction B1 [1]
- (ii)** charge B1 [1]
- (b) (i)**  $\Sigma E = \Sigma IR$  C1  
 $20 - 12 = 2.0(0.6 + R)$  *(not used 3 resistors 0/2)* A1 [2]  
 $R = 3.4\Omega$
- (ii)**  $P = EI$  C1  
 $= 20 \times 2$   
 $= 40 \text{W}$  A1 [2]
- (iii)**  $P = I^2R$  C1  
 $P = (2)^2 \times (0.1 + 0.5 + 3.4)$   
 $= 16 \text{W}$  A1 [2]
- (iv)** efficiency = useful power / output power C1  
 $24 / 40 = 0.6$  or  $12 \times 2 / 20 \times 2$  or 60% A1 [2]

**Q25.**



<b>6</b>	<b>(a)</b>	<b>(i)</b> chemical to electrical	B1	[1]
		<b>(ii)</b> electrical to thermal / heat or heat and light	B1	[1]
	<b>(b)</b>	<b>(i)</b> $P_B = EI$ or $I^2(R_1 + R_2)$	A1	[1]
		<b>(ii)</b> $P_R = I^2R_1$	A1	[1]
	<b>(c)</b>	$R = \rho l / A$ or clear from the following equation ratio = $I^2R_1 / I^2R_2 = \frac{\rho l / \pi d^2}{\rho(2l) / \pi(2d)^2}$ or $R_1$ has 8× resistance of $R_2$ = 8 or 8:1	B1 C1 A1	[1] [1] [3]
	<b>(d)</b>	$P = V^2 / R$ or $E^2 / R$ (V or E the same) hence ratio is 1/8 or 1:8 = 0.125 (allow ecf from (c))	C1 A1	[2]

Q26.

<b>6</b>	<b>(a)</b>	charge = current × time	B1	[1]
	<b>(b)</b>	<b>(i)</b> $P = V^2 / R$ $= (240)^2 / 18 = 3200W$	C1 A1	[2]
		<b>(ii)</b> $I = V / R = 240 / 18 = 13.3A$	A1	[1]
		<b>(iii)</b> charge = $It = 13.3 \times 2.6 \times 10^6$ $= 3.47 \times 10^7 C$	C1 A1	[2]
		<b>(iv)</b> number of electrons = $3.47 \times 10^7 / 1.6 \times 10^{-19} (= 2.17 \times 10^{26})$ number of electrons per second = $2.17 \times 10^{26} / 2.6 \times 10^6 = 8.35 \times 10^{19}$	C1 A1	[2]

Q27.

<b>6</b>	<b>(a)</b>	p.d. = <u>work done / energy transformed</u> (from electrical to other forms) charge	B1	[1]
	<b>(b)</b>	<b>(i)</b> maximum 20V	A1	[1]
		<b>(ii)</b> minimum = $(600 / 1000) \times 20$ $= 12V$	C1 A1	[2]
	<b>(c)</b>	<b>(i)</b> use of $1.2k\Omega$ $1/1200 + 1/600 = 1/R$ , $R = 400\Omega$	M1 A1	[2]
		<b>(ii)</b> total parallel resistance ( $R_2 + LDR$ ) is less than $R_2$ (minimum) p.d. is reduced	M1 A1	[2]

Q28.



- 6 (a) (i) arrow in upward direction, foot near P ..... B1
- (ii) curved path consistent with (i) between plates ..... B1  
then straight (with no kink at change-over) ..... B1 [3]
- (b)  $E = V/d$  ..... C1  
 $= 400 / (0.8 \times 10^{-2})$   
 $= 5.0 \times 10^4 \text{ V m}^{-1}$  ..... (allow 1 sig fig) ..... A1 [2]
- (c) (i)  $F = Eq$  ..... C1  
 $= 5.0 \times 10^4 \times 1.6 \times 10^{-19}$   
 $= 8.0 \times 10^{-15} \text{ N}$  ..... (allow 1 sig fig and e.c.f.) ..... A1
- (ii)  $a = F/m$  ..... C1  
 $= (8.0 \times 10^{-15}) / (9.1 \times 10^{-31})$   
 $= 8.8 \times 10^{15} \text{ m s}^{-2}$  ..... (allow 1 sig fig and e.c.f.) ..... A1 [4]
- (d) because  $F_E$  is normal to horizontal motion ..... M1  
no effect ..... A1 [2]

Q29.

- 7 (a) (i) e.m.f. = energy / charge ..... C1  
 $= (1.6 \times 10^5) / (1.8 \times 10^4)$   
 $= 8.9 \text{ V}$  ..... A1
- (ii) current =  $\Delta Q / \Delta t$  ..... C1  
 $= (1.80 \times 10^4) / (1.3 \times 10^5)$   
 $= 0.14 \text{ A}$  ..... A1 [4]
- (b) (i) energy  $\propto R$  (or formula) ..... C1  
energy =  $(15 / 45) \times 1.14 \times 10^5$  ..... C1  
 $= 3.7 \times 10^4 \text{ J}$  ..... A1
- (ii) energy dissipated in internal resistance (of battery) ..... B1 [4]  
OR in extra resistance in circuit

Q30.



- 5 (a) (i) arrow from B towards A ..... B1
- (ii)  $E = V/d$   
 $= 450/(9.0 \times 10^{-2})$  ..... C1  
 $= 5.0 \times 10^3 \text{ N C}^{-1}$  (accept 1 sig. fig) ..... A1 [3]
- (b) (i) energy  $= qV$  or  $Eqd$  ..... C1  
 $= 1.6 \times 10^{-19} \times 450$  ..... A1  
 $= 7.2 \times 10^{-17} \text{ J}$  ..... A0
- (ii)  $E_k = \frac{1}{2}mv^2$   
 $7.2 \times 10^{-17} = \frac{1}{2} \times 9.1 \times 10^{-31} \times v^2$  ..... C1  
 $v = 1.26 \times 10^7 \text{ m s}^{-1}$  ..... A1 [4]
- (c) line from origin, curved in correct direction but not 'level out' ..... B1 [1]

Q31.

- 7 (a) (i)  $P = Vi$  ..... C1  
 $1200 = 240 \times i$  ..... M1  
 $i = 5.0 \text{ A}$  ..... A0 [4]
- (ii)  $V = iR$   
 $240 = 5.0 \times R$  ..... C1  
 $R = 48\Omega$  ..... A1
- (b) (i) p.d.  $= (5.0 \times 4.0 =) 20 \text{ V}$  ..... A1  
(ii) mains voltage  $= (240 + 20 =) 260 \text{ V}$  ..... A1  
(iii)  $P = (20 \times 5.0 =) 100 \text{ W}$  ..... A1 [3]
- (c) power input  $= 1200 + 100 = 1300 \text{ W}$  ..... C1  
efficiency  $= 1200/1300 = 0.92$  ..... A1 [2]

Q32.



6	(a) (i)	resistance is ratio $V/I$ (at a point) <i>either gradient increases or I increases more rapidly than V</i>	B1 B1 [2]
		<i>(If states <math>R = \text{reciprocal of gradient}</math>, then 0/2 marks here)</i>	
	(ii)	current = 2.00 mA	C1
		resistance = 2 000 $\Omega$	A1 [2]
	(b) (i)	straight line from origin	M1
		passing through (6.0 V, 4.0 mA) (allow $\frac{1}{2}$ square tolerance)	A1 [2]
	(ii)	individual currents are 0.75 mA and 1/33 mA	C1
		current in battery = 2.1 mA	A1 [2]
		<i>(allow argument in terms of <math>P = I^2R</math> or <math>IV</math>)</i>	
	(c)	same current in R and in C	M1
		p.d. across C is larger than that across R	M1
		so since power = $VI$ , greater in C	A1 [3]
		<i>(allow argument in terms of <math>P = I^2R</math> or <math>IV</math>)</i>	

## Q33.

6	(a)	force must be upwards (on positive charge) so plate Y is positive	M1 A1 [2]
	(b) (i)	$E = V/d$ $= 630/(0.75 \times 10^{-2})$ $= 8.4 \times 10^4 \text{ N C}^{-1}$	C1 A1 [2]
	(ii)	$qE = mg$ $q = (9.6 \times 10^{-15} \times 9.8) / (8.4 \times 10^4)$ $= 1.12 \times 10^{-18} \text{ C}$	C1 C1 A1 [3]

## Q34.

7	(a)	<i>either</i> $V = E R_1 / (R_1 + R_2)$ <i>or</i> $I = E / (R_1 + R_2)$ $= \frac{1800}{3000} \times 4.50$ $= 2.70 \text{ V}$	C1 M1 A0 [2]
	(b) (i)	for a wire, $V = I \times (\rho L/A)$ $I, \rho$ and $A$ are constant so $V \propto L$	M1 A1 A0 [2]

(ii) 1 2.70 V A1 [1]

$$2 \frac{L}{100} = \frac{2.70}{4.50}$$
C1

$$L = 60.0 \text{ cm}$$
A1 [2]

(iii) thermistor resistance decreases as temperature rises so QM is shorter M1  
A1 [2]

Q35.

- 7 (a) both measure (energy / work) / charge for e.m.f., transfer of chemical energy to electrical energy for p.d., transfer of electrical energy to thermal energy / other forms B1  
B1  
B1 [3]
- (b) (i)  $I_1 + I_2 = I_3$  B1 [1]  
 (ii) 1.  $E_2 = I_2 R_2 + I_3 R_3$  B1 [1]  
 2.  $E_1 - E_2 = I_1 R_1 - I_2 R_2$  B1 [1]

Q36.

6 (a) power =  $VI$   
 current =  $10.5 \times 103 / 230$   
 $= 45.7 \text{ A}$

C1  
M1  
A0 [2]

(b) (i) p.d. across cable = 5.0 V C1  
 $R = 5.0 / 46$  C1  
 $= 0.11 \Omega$  A1 [3]

(ii)  $R = \rho L / A$  C1  
 $0.11 = (1.8 \times 10^{-8} \times 16 \times 2) / A$  C1  
 $A = 5.3 \times 10^{-6} \text{ m}^2$  A1 [3]

(wires in parallel, not series, allow max 1/3 marks)

(c) (i) either power =  $V^2 / R$  or power  $\propto V^2$  C1  
 ratio =  $(210 / 230)^2 = 0.83$  A1 [2]

(ii) resistance of cable is greater  
 greater power loss/fire hazard/insulation may melt  
 wire may melt/cable gets hot M1  
A1 [2]

Q37.

- 4 (a) (i) either force =  $e \times (V / d)$  or  $E = V/d$  C1  
 $= 1.6 \times 10^{-19} \times (250 / 7.6 \times 10^{-3})$  C1  
 $= 5.3 \times 10^{-15} \text{ N}$  A1 [3]
- (ii) either  $\Delta E_k = eV$  or  $\Delta E_k = Fd$  C1  
 $= 1.6 \times 10^{-19} \times 250$  M1  
 $= 5.3 \times 10^{-15} \times 7.6 \times 10^{-3}$  A0 [2]
- (allow full credit for correct working via calculation of  $a$  and  $v$ )



# MEGA LECTURE

- (iii) either  $\Delta E_K = \frac{1}{2}mv^2$   
 $4.0 \times 10^{-17} = \frac{1}{2} \times 9.1 \times 10^{-31} \times v^2$   
 $v = 9.4 \times 10^6 \text{ m s}^{-1}$  C1  
 or  $v^2 = 2as$  and  $a = F/m$   
 $v^2 = (2 \times 5.3 \times 10^{-15} \times 7.6 \times 10^{-3}) / (9.11 \times 10^{-31})$  (C1)  
 $v = 9.4 \times 10^6 \text{ m s}^{-1}$  (A1)
- (b) speed depends on (electric) potential difference M2  
*(If states  $\Delta E_K$  does not depend on uniformity of field, then award 1 mark, treated as an M mark)*  
 so speed always the same A1 [3]

Q38.

- 7 (a) either  $V = IP$  B1  
 current in circuit =  $E / (P + Q)$  B1  
 hence  $V = EP / (P + Q)$  A0 [2]  
 or current is the same throughout the circuit (M1)  
 $V/P = E/(P+Q)$  (A1)  
 hence  $V = EP / (P + Q)$  (A0)
- (b) (i) (as temperature rises), resistance of (thermistor) decreases M1  
 either resistance of parallel combination decreases  
 or p.d. across 5 kΩ resistor / thermistor decreases M1  
 p.d. across 2000 Ω resistor / voltmeter reading increases A1 [3]
- (ii) if  $R$  is the resistance of the parallel combination,  
 either  $3.6 = (2 \times 6) / (2 + R)$  or current in 2 kΩ resistor = 1.8 mA C1  
 $R = 1.33 \text{ k}\Omega$  current in 5 kΩ resistor = 0.48 mA C1  
 $\frac{1}{1.33} = \frac{1}{5} + \frac{1}{T}$  current in thermistor = 1.32 mA C1  
 $T = 1.82 \text{ k}\Omega$   $T = 2.4 / 1.32 = 1.82 \text{ k}\Omega$  A1 [4]

Q39.

- 6 (a) energy transferred from source / changed from some form to electrical ..... M1  
 per unit charge (to drive charge round a complete circuit) ..... A1 [2]
- (b) and power in  $R = I^2X$  ..... M1  
 $E = I(X + r)$  ..... M1  
 power in cell =  $EI$  and algebra clear leading to ratio =  $X / (X + r)$  ..... A1 [3]



(c) (i) 1.4 W ..... A1  
 $0.40 \Omega$  ..... (allow  $\pm 0.05 \Omega$ ) ..... A1 [2]

(ii) current in circuit =  $\sqrt{1.4/0.4} = 1.87$  A ..... C1  
 $1.5 = 1.87(r + 0.40)$  ..... C1  
 $r = 0.40 \Omega$  ..... A1 [3]

(d) either less power lost / energy wasted / lost  
or greater efficiency (of energy transfer) ..... B1 [1]

[Total: 11]

## Q40.

6 (a) total resistance in series =  $2R$   
total resistance in parallel =  $\frac{1}{2}R$  ..... M1  
ratio is  $2R / \frac{1}{2}R = 4$  ..... (allow mark if clear numbers in the ratio) ..... A0 [1]

(b) at 1.5 V, current is 0.10 A ..... C1  
resistance =  $V/I = \frac{1.5}{0.1}$   
=  $15 \Omega$  ..... A1 [2]  
(use of tangent or any other current scores no marks)

(c)

	p.d. across each lamp / V	resistance of each lamp / $\Omega$	combined resistance / $\Omega$
series	1.5	15	30
parallel	3.0	20	10

column 1 ..... A1  
columns 2 and 3: max 3 marks with -1 mark for each error or omission ..... A3 [4]

(d) (i) ratio is 3 ..... (allow e.c.f.) ..... A1 [1]  
(ii) resistance increases as potential difference increases ..... B1  
increasing p.d. increases current ..... B1  
current increases non-linearly so resistance increases ..... B1 [3]

[Total: 11]

## Q41.



<b>6 (a) (i)</b>	either $P = V^2 / R$ or $R = 4.0 \Omega$	C1 A1	[2]
<b>(ii)</b>	sketch vertical axis labelled appropriately (straight) line from origin then curved in correct direction line passes through 12 V, 3.0 A	B1 B1 B1	[3]
<b>(b) (i)</b>	2.0 kW	A1	[1]
<b>(ii)</b>	0.5 kW	A1	[1]
<b>(iii)</b>	total resistance = $3R / 2$ power = 0.67 kW	C1 A1	[2]

**Q42.**

<b>6 (a) (i)</b>	at $22.5^\circ\text{C}$ , $R_T = 1600\Omega$ or $1.6\text{k}\Omega$ total resistance = $800\Omega$	C1 A1	[2]
<b>(ii)</b>	either use of potential divider formula or current = $9 / 2000$ (4.5 mA) $V = (0.8/2.0) \times 9$ = 3.6V	C1 A1	[2]
<b>(b) (i)</b>	total resistance = $4/5 \times 1200$ = $960\Omega$	C1 A1	[2]
<b>(ii)</b>	for parallel combination, $1/960 = 1/1600 + 1/R_T$ $R_T = 2400\Omega$ / $2.4\text{k}\Omega$ temperature = $11^\circ\text{C}$	C1 A1	[2]
<b>(c)</b>	e.g. only small part of scale used / small sensitivity non-linear (any two sensible suggestions, 1 each, max 2)	B1 B1	[2]

**Q43.**


**MEGA LECTURE**

<b>7 (a) (i)</b>	path: reasonable curve upwards between plates straight and at a tangent to the curve beyond the plates	B1 B1 [2]
<b>(ii) 1.</b>	$F = E.g$	B1 [1]
<b>2.</b>	$t = L/v$	B1 [1]
<b>(b) (i)</b>	total momentum of a system remains constant <b>or</b> total momentum of a system before a collision equals total momentum after collision provided no external force acts on the system (do not accept 'conserved' but otherwise correct statement gets 1/2)	M1 A1 [2]
<b>(ii)</b>	$\Delta p = EqL/v$ allow ecf from (a)(ii)	B1 [1]
<b>(iii) either</b>	charged particle is not an isolated system so law does not apply	M1 A1 [2]
<b>or</b>	system is particle and 'plates' equal and opposite $\Delta p$ on plates / so law applies	(M1) (A1)

**Q44.**

<b>8 (a) (i)</b>	<b>either</b> $P = V^2/R$ or $I = 1200/230$ or 5.22 $R = (230 \times 230)/1200$ $= 230^2/1200$ $= 44.1\Omega$	$R = 230/5.22$ $= 44.1\Omega$	C1 M1 A0 [2]
<b>(ii)</b>	$R = \rho L/A$ $= (1.7 \times 10^{-8} \times 9.2 \times 2) / (\pi \times \{0.45 \times 10^{-3}\}^2)$ $= 0.492\Omega$		C1 M1 A0 [2]
<b>(b)</b>	current = $230/44.6$ power = $(230/44.6)^2 \times 44.1$ = 1170 W <i>(allow full credit for solution based on potential divider)</i>		C1 C1 A1 [3]
<b>(c)</b>	e.g. less power dissipated in the heater / smaller p.d. across heater / more power loss in cable / current lower cable becomes heated / melts <i>(any two sensible suggestions, 1 each, max 2)</i>		B1 B1 [2]

**Q45.**



5 (a) ohm = volt / ampere	B1 [1]
(b) $\rho = RA / l$ or unit is $\Omega \text{m}$ units: $\text{V} \cdot \text{A}^{-1} \text{m}^2 \text{m}^{-1} = \text{Nm} \cdot \text{C}^{-1} \text{A}^{-1} \text{m}^2 \text{m}^{-1}$ $= \text{kg} \cdot \text{m}^2 \cdot \text{s}^{-2} \cdot \text{A}^{-1} \cdot \text{s}^{-1} \cdot \text{A}^{-1} \cdot \text{m}^2 \cdot \text{m}^{-1}$ $= \text{kg} \cdot \text{m}^3 \cdot \text{s}^{-3} \cdot \text{A}^{-2}$	C1 C1 A1 [3]
(c) (i) $\rho = [3.4 \times 1.3 \times 10^{-7}] / 0.9$ $= 4.9 \times 10^{-7} (\Omega \text{m})$	C1 A1 [2]
(ii) max = $2.(0) \text{ V}$ min = $2 \times (3.4 / 1503.4) = 4.5 \times 10^{-3} \text{ V}$	A1 A1 [2]
(iii) $P = V^2 / R$ or $P = VI$ and $V = IR$ $= (2)^2 / 3.4$ $= 1.18$ (allow 1.2) W	C1 A1 [2]
(d) (i) power in Q is zero when $R = 0$	B1 [1]
(ii) power in Q = 0 / tends to zero as $R = \infty$	B1 [1]

**Q46.**

4 (a) electric field strength = force / positive charge	B1 [1]
(b) (i) at least three equally spaced parallel vertical lines direction down	B1 B1 [2]
(ii) $E = 1500 / 20 \times 10^{-3} = 75000 \text{ V m}^{-1}$	A1 [1]
(iii) $F = qE$ ( $W = mq$ and) $qE = mq$ $q = mq / E = 5 \times 10^{-15} \times 9.81 / 75000$ $= 6.5 \times 10^{-19} \text{ C}$ negative charge	C1 C1 A1 A1 [4]
(iv) $F > mg$ or $F$ now greater drop will move <u>upwards</u>	B1 B1 [2]

**Q47.**

5 (a) (i) $I_1 + I_3 = I_2$	A1 [1]
(ii) $E_1 = \frac{I_2 R_2}{2} + \frac{I_1 R_2}{2} + I_1 R_1 + I_1 r_1$	A1 [1]
(iii) $E_1 - E_2$ $= -I_3 r_2 + I_1 (R_1 + r_1 + R_2 / 2)$	B1 B1 [2]
(b) p.d. across <u>BJ</u> of wire changes / resistance of <u>BJ</u> changes there is a difference in p.d. across wire and p.d. across cell $E_2$	B1 B1 [2]



048.

- |     |  |              |
|-----|--|--------------|
| 4   | (a) $p.d. = \frac{\text{energy transformed from electrical to other forms}}{\text{unit charge}}$ | B1           |
|     | e.m.f. = $\frac{\text{energy transformed from other forms to electrical}}{\text{unit charge}}$   | B1 [2]       |
| (b) | (i) sum of e.m.f.s (in a closed circuit) = sum of potential differences                          | B1 [1]       |
|     | (ii) $4.4 - 2.1 = I \times (1.8 + 5.5 + 2.3)$<br>$I = 0.24 \text{ A}$                            | M1<br>A1 [2] |
|     | (iii) arrow (labelled) $I$ shown anticlockwise   | A1 [1]       |
|     | (iv) 1. $V = I \times R = 0.24 \times 5.5 = 1.3(2)\text{V}$                                      | A1 [1]       |
|     | 2. $V_A = 4.4 - (I \times 2.3) = 3.8(5)\text{V}$   | A1 [1]       |
|     | 3. either $V_B = 2.1 + (I \times 1.8)$ or $V_B = 3.8 - 1.3 = 2.5(3)\text{V}$                     | C1<br>A1 [2] |

**Q49.**

- |     |  |                |     |
|-----|--|----------------|-----|
| 2   | (a) resistance = potential difference / current  | B1             | [1] |
|     | (b) (i) metal wire in series with power supply and ammeter<br>voltmeter in parallel with metal wire<br>rheostat in series with power supply or potential divider arrangement<br>or variable power supply | B1             | [1] |
|     | (ii) 1. intercept on graph<br>2. scatter of readings about the best fit line   | B1             | [1] |
|     | (iii) correction for zero error explained<br>use of V and corrected I values from graph<br>resistance = $V/I = 22.2(2)\Omega$ [e.g. $4.0 / 0.18$ ]   | B1<br>C1<br>A1 | [3] |
| (c) | $R = 6.8 / 0.64 = 10.625$  | C1             |     |
|     | $\%R = \%V + \%I$<br>$= (0.1 / 6.8) \times 100 + (0.01 / 0.64) \times 100$<br>$= 1.47\% + 1.56\%$  | C1             |     |
|     | $\Delta R = 0.0303 \times 10.625 = 0.32\Omega$   |                |     |
|     | $R = 10.6 \pm 0.3\Omega$   | A1             | [3] |

**Q50.**

- 5 (a) (i)**  $I_1 = I_2 + I_3$  B1 [1]
- (ii)**  $I = V / R$  or  $I_2 = 12 / 10 (= 1.2 \text{ A})$  C1  
 $R = [1/6 + 1/10]^{-1}$  [total  $R = 3.75 \Omega$ ] or  $I_3 = 12 / 6 (= 2.0 \text{ A})$  C1  
 $I_1 = 12 / 3.75 = 3.2 \text{ A}$  or  $I_1 = 1.2 + 2.0 = 3.2 \text{ A}$  A1 [3]
- (iii)** power =  $VI$  or  $I^2R$  or  $V^2/R$  C1  
 $x = \frac{\text{power in wire}}{\text{power in series resistors}} = \frac{I_2^2 R_w}{I_3^2 R_s}$  or  $\frac{V_2}{V_3}$  or  $\frac{V^2 / R_w}{V^2 / R_s}$  C1  
 $x = 12 \times 1.2 / 12 \times 2.0 = 0.6(0)$  allow 3 / 5 or 3:5 A1 [3]
- (b)** p.d. BC:  $12 - 12 \times 0.4 = 7.2 (\text{V})$  / p.d. AC =  $4.8 (\text{V})$  C1  
p.d. BD:  $12 - 12 \times 4 / 6 = 4.0 (\text{V})$  / p.d. AD =  $8.0 (\text{V})$  C1  
p.d. =  $3.2 \text{ V}$  A1 [3]

**Q51.**

- 4 (a)** e.m.f. = chemical energy to electrical energy M1  
p.d. = electrical energy to thermal energy M1  
idea of per unit charge A1 [3]
- (b)**  $E = I(R+r)$  or  $I = E/(R+r)$  (any subject) B1 [1]
- (c) (i)**  $E = 5.8 \text{ V}$  B1 [1]  
**(ii)** evidence of gradient calculation or calculation with values from graph C1  
e.g.  $5.8 = 4 + 1.0 \times r$  A1 [2]  
 $r = 1.8 \Omega$
- (d) (i)**  $P = VI$  C1  
 $P = 2.9 \times 1.6 = 4.6 (4.64) \text{ W}$  A1 [2]
- (ii)** power from battery =  $1.6 \times 5.8 = 9.28$  or efficiency =  $VI/EI$  C1  
efficiency =  $(4.64 / 9.28) \times 100 = 50\%$  or  $(2.9 / 5.8) \times 100 = 50\%$  A1 [2]

**Q52.**

- 6 (a)** p.d. = work (done) / charge OR energy transferred from (electrical to other forms) / (unit) charge B1 [1]
- (b) (i)**  $R = \rho l / A$  C1  
 $\rho = 18 \times 10^{-9}$  C1  
 $R = (18 \times 10^{-9} \times 75) / 2.5 \times 10^{-6} = 0.54 \Omega$  A1 [3]
- (ii)**  $V = IR$  C1  
 $R = 38 + (2 \times 0.54)$  C1  
 $I = 240 / 39.08 = 6.1 (6.14) \text{ A}$  A1 [3]


**MEGA LECTURE**

(iii)  $P = I^2R$  or  $P = VI$  and  $V = IR$  or  $P = V^2/R$  and  $V = IR$   
 $= (6.14)^2 \times 2 \times 0.54$   
 $= 41 (40.7)$  W

C1	
C1	
A1	[3]

- (c) area of wire is less (1/5) hence resistance greater (x5)  
OR  $R \propto 1/A$  therefore  $R$  is greater  
p.d. across wires greater so power loss in cables increases
- |    |     |
|----|-----|
| M1 |     |
| A1 | [2] |

Q53.

- 6 (a) e.m.f. = total energy available (per unit charge)  
some (of the available energy) is used/lost/wasted/given out in the internal resistance of the battery (hence p.d. available less than e.m.f.)
- |    |     |
|----|-----|
| B1 |     |
| B1 | [2] |
- (b) (i)  $V = IR$   
 $I = 6.9 / 5.0 = 1.4$  (1.38) A
- |    |     |
|----|-----|
| C1 |     |
| A1 | [2] |
- (ii)  $r = \text{lost volts} / \text{current}$   
 $= (9 - 6.9) / 1.38 = 1.5$ (2)  $\Omega$
- |    |     |
|----|-----|
| C1 |     |
| A1 | [2] |
- (c) (i)  $P = EI$  (not  $P = VI$  if only this line given or 9 V not used in second line)  
 $= 9 \times 1.38 = 12$  (12.4) W
- |    |     |
|----|-----|
| C1 |     |
| A1 | [2] |
- (ii) efficiency = output power / total power  
 $= VI / EI = 6.9 / 9$  or  $(9.52) / (12.4) = 0.767 / 76.7\%$
- |    |     |
|----|-----|
| C1 |     |
| A1 | [2] |

Q54.

- 7 (a) (i) six vertical lines from plate to plate equally spaced across plates  
[only allow if greatest to least spacing is < 1.3, condone slight curving on the two edges. There must be no area between the plates where an additional line(s) could be added.]  
arrow downwards on at least one line
- |    |     |
|----|-----|
| B1 |     |
| B1 | [2] |
- (ii)  $E = V/d$   
 $= 1200 / 40 \times 10^{-3} = 3.0 \times 10^4$   $\text{Vm}^{-1}$  (allow 1 s.f.)
- |    |     |
|----|-----|
| C1 |     |
| A1 | [2] |
- (b) (i)  $F = Ee$   
 $= 3 \times 10^4 \times 1.6 \times 10^{-19} = 4.8 \times 10^{-15}$  N
- |    |     |
|----|-----|
| C1 |     |
| A1 | [2] |
- (ii) couple =  $F \times \text{separation of charges}$   
 $= 4.8 \times 10^{-15} \times 15 \times 10^{-3} = 7.2 \times 10^{-17}$   
unit: N m or unit consistent with unit used for the separation
- |    |     |
|----|-----|
| C1 |     |
| A1 |     |
| B1 | [3] |
- (iii) A at top/next to +ve plate B at bottom/next to -ve plate vertically aligned  
[could be shown on the diagram]  
forces are equal and opposite in same line / no resultant force and no resultant torque
- |    |     |
|----|-----|
| M1 |     |
| A1 | [2] |





www.megalecture.com

whatsapp: +92 323 509 4443, email: megalecture@gmail.com

