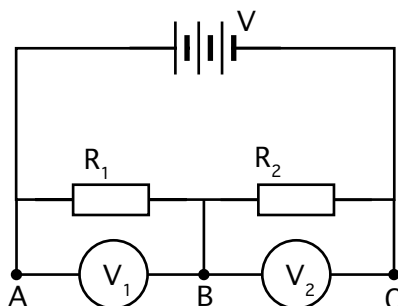


### Potential dividers

Name & Set

- 1 In the circuit shown below the p.d. of the battery is 12 V. Assume that the battery has no internal resistance



If  $R_1$  is  $50\Omega$  and  $R_2$  is  $250\Omega$

- (i) what would voltmeter  $V_1$  read?

---



---



---

[3]

- (ii) what would voltmeter  $V_2$  read?

---

[1]

- (iii) what is the voltage at A? \_\_\_\_\_ [1]


- (iv) what is the voltage at B? \_\_\_\_\_ [1]

- (v) What is the voltage at C? \_\_\_\_\_ [1]

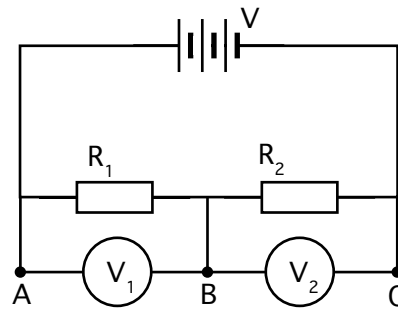- (vi) Plot a graph of the p.d. across each part of the circuit from the positive terminal of the cell (+) to the negative terminal of the cell (-). BB on the graphs represents the wire between  $R_1$  &  $R_2$  is. [3]



- 2 In the circuit shown below the p.d. of the battery is 36 V. Assume that the battery has no internal resistance



If  $R_1$  is  $10\text{K}\Omega$  and  $R_2$  is  $80\text{K}\Omega$

- (i) What would voltmeter  $V_1$  read?

---



---



---

[3]

- (ii) What would voltmeter  $V_2$  read? \_\_\_\_\_ [1]

- (iii) what is the voltage at A? \_\_\_\_\_ [1]

- (iv) what is the voltage at B? \_\_\_\_\_ [1]

- (v) What is the voltage at C? \_\_\_\_\_ [1]

- (vi) What current is drawn from the battery?

---




---




---

[3]

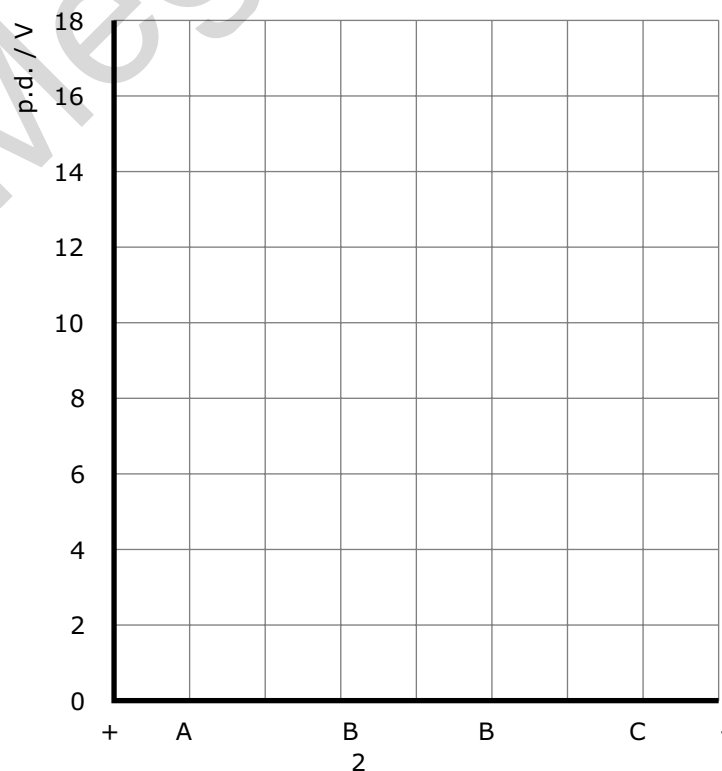(vii) Plot a graph of the pd around the circuit. [3]



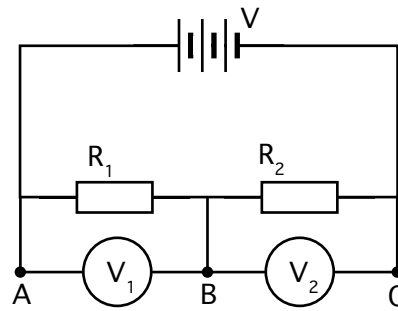- 3 In the circuit shown below the p.d. of the battery is 6 V. Assume that the battery has no internal resistance



If  $R_1$  is  $250\text{K}\Omega$  and  $R_2$  is  $500\text{K}\Omega$ ,

- (i) What would voltmeter  $V_1$  read?

---

---

---

[3]

- (ii) What would voltmeter  $V_2$  read?

---

---

---

[3]

- (iii) What is the voltage at A? \_\_\_\_\_ [1]

- (iv) What is the voltage at B? \_\_\_\_\_ [1]

- (v) What is the voltage at C? \_\_\_\_\_ [1]

- (vi) What current is drawn from the battery?


---

---

---

[3]

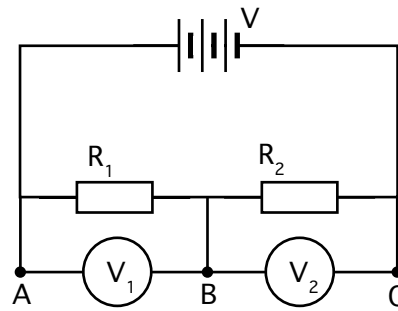- 4 In the circuit shown below the p.d. of the battery is 18 V. Assume that the battery has no internal resistance



If  $R_1$  is  $600\text{k}\Omega$  and  $R_2$  is  $300\text{k}\Omega$

- (i) What would voltmeter  $V_1$  read?

---

---

---

[3]

- (ii) What would voltmeter  $V_2$  read?

---

---

---

[3]

- (iii) What is the voltage at A? \_\_\_\_\_ [1]

- (iv) What is the voltage at B? \_\_\_\_\_ [1]

- (v) What is the voltage at C? \_\_\_\_\_ [1]

- (vi) What current is drawn from the battery?


---

---

---

[3]

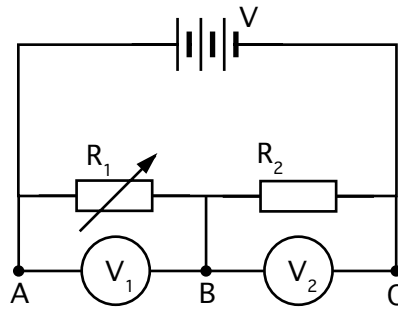- 5 In the circuit shown below the p.d. of the battery is 15 V. Assume that the battery has no internal resistance



$R_1$  is a variable resistor that varies from  $0\Omega$  to  $500\Omega$  and  $R_2$  is  $100\Omega$

- (i) What would voltmeter  $V_1$  read when  $R_1$  is set to its lowest resistance?

\_\_\_\_\_ [1]

- (ii) What would voltmeter  $V_2$  read when  $R_1$  is set to its lowest resistance??

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_ [3]

- (iii) What would voltmeter  $V_1$  read when  $R_1$  is set to its highest resistance?

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_ [3]

- (iv) What would voltmeter  $V_2$  read when  $R_1$  is set to its highest resistance?

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_ [3]


- (v) What should the resistance of  $R_1$  be if voltmeter  $V_1$  read 6V?

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_ [3]

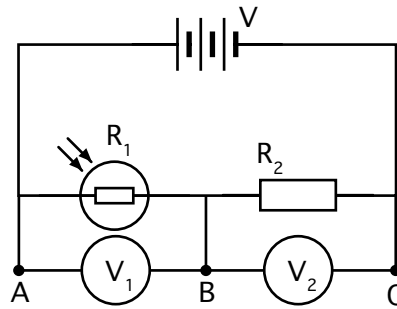- (iv) What should the resistance of  $R_1$  be if voltmeter  $V_2$  read 10V?

\_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_ [3]

- 5 In the circuit shown below the p.d. of the battery is 10 V. Assume that the battery has no internal resistance



$R_1$  is an LDR that varies from  $0\Omega$  in full light to  $1000\Omega$  in the dark and  $R_2$  is a fixed resistor of  $100\Omega$

- (i) What would voltmeter  $V_1$  read when the LDR is covered over so no light reaches it?

---



---



---

[3]

- (ii) What would voltmeter  $V_2$  read when the LDR is covered over so no light reaches it?

---

[1]

- (iii) What would voltmeter  $V_1$  read when the LDR is fully illuminated?

---

[1]

- (iv) What would voltmeter  $V_2$  read when LDR is fully illuminated?

---

[1]

- (ii) What should the resistance of  $R_1$  be if voltmeter  $V_1$  read 2.5V?

---



---



---

[3]

- (ii) What should the resistance of  $R_1$  be if voltmeter  $V_2$  read 2.5V?

---



---




---

[3]

- 6 The circuit diagram below shows a type of electric thermometer. A thermistor,  $R_T$ , is used as a temperature probe. A high resistance voltmeter is used to indicate the temperature. Your task is to draw up a calibration curve for the voltmeter so that it can be read directly as a thermometer.

Data for the resistance of the thermistor,  $R_T$ , as a function of its temperature is given in the table. The value of the fixed resistor  $R_R$  is  $1\text{ k}\Omega$ .

Temp ( $^{\circ}\text{C}$ )	$R_T$ ( $\text{k}\Omega$ )
10	2.1
20	1.4
30	1.0
40	0.7
50	0.5
60	0.3

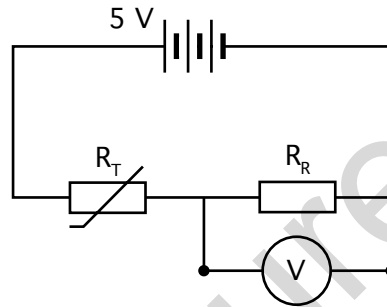

- (a) Plot a graph of temperature against resistance for the thermistor over the range  $0^{\circ}\text{C}$  to  $100^{\circ}\text{C}$ . (Use **Graphical Analysis** or **Excel** if you wish and submit the print out.) [3]



(b) Use the graph and a calculation to determine what the voltmeter will read when the thermistor is at 30°C.


\_\_\_\_\_ [2]

(c) Draw up a table of the p.d. across the resistance  $R_R$  corresponding to different thermistor temperatures. (Use **Graphical Analysis** or **Excel** if you wish and submit the print out.)

\_\_\_\_\_  
 \_\_\_\_\_ [4]

Temperature / °C	0	10	20	30	40	50	60	70	80	90	100
p.d. / Volts											

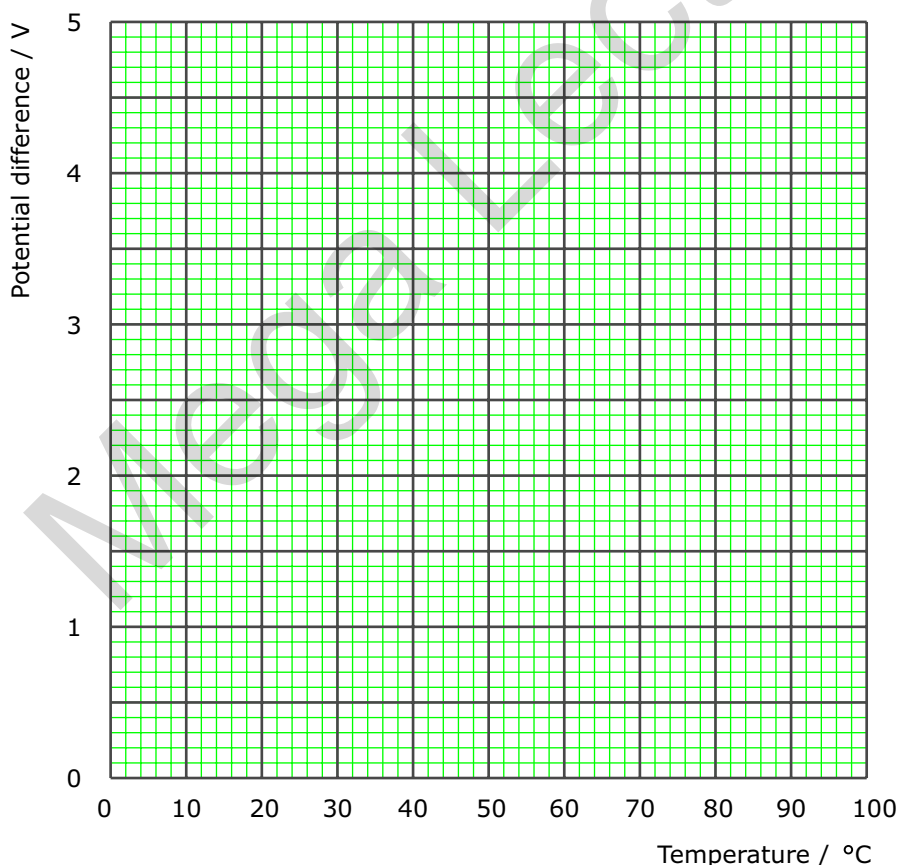(d) Draw a graph of voltmeter reading (on y axis) against temperature of thermistor (on the x axis).



(e) What does the voltmeter read at

0 °C \_\_\_\_\_ 70 °C \_\_\_\_\_ 100 °C? \_\_\_\_\_ [3]

(f) Between what temperatures is the thermometer scale linear? \_\_\_\_\_ [1]