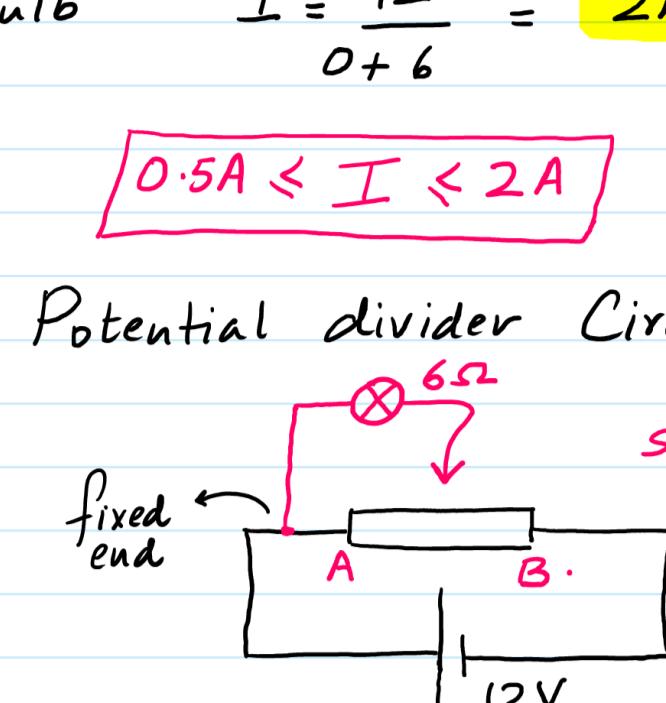


28 February 2021 17:02

Comparison b/w a Variable Resistor Circuit & a potential divider circuits.

① Variable Resistor Circuit




(i) Cal minimum Current in the Bulb $I = \frac{12}{18+6} = 0.5A$

(ii) Cal maximum Current in the Bulb $I = \frac{12}{6} = 2A$

$$0.5A \leq I \leq 2A$$

② Potential divider Circuit.

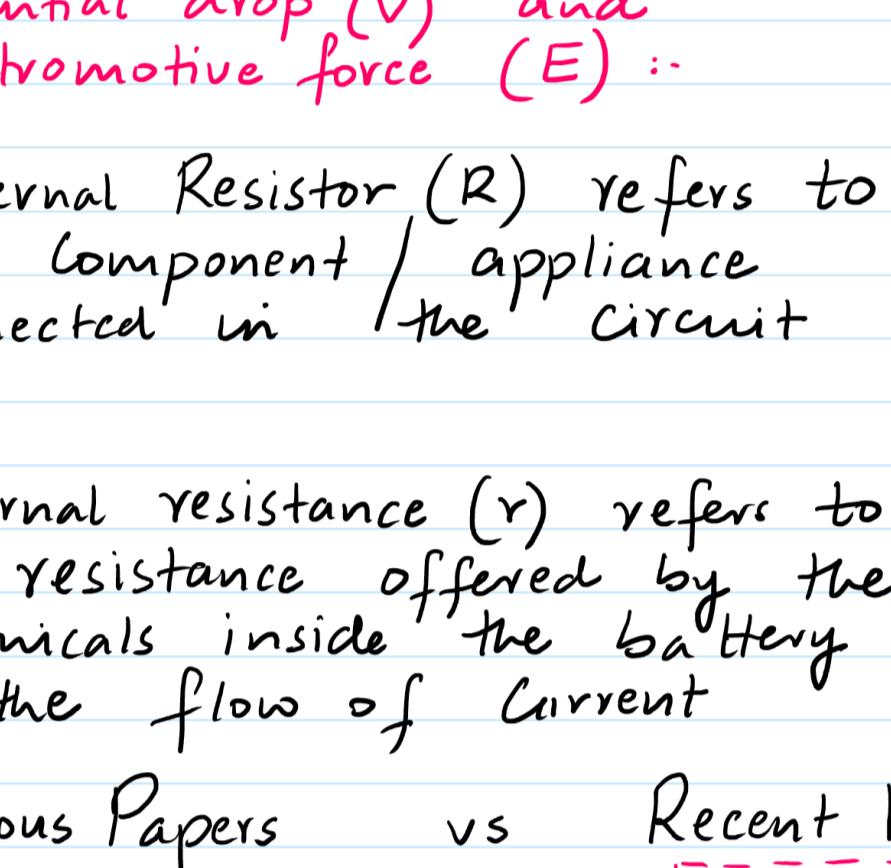

(i) Cal the Current in the Bulb

when Sliding Contact is placed at B
Bulb gets 12V; $R = 6\Omega$.

$$I = \frac{12}{6} = 2A$$

(ii) Cal. the Current in the Bulb when the Sliding Contact is placed at A
Bulb gets 0V; $R = 6\Omega$.

$$I = \frac{0}{6} = 0A$$

$$0A \leq I \leq 2A$$


Note: Both circuits can be used to adjust the brightness of the bulb however a potential divider circuit provides a wider range of current i.e. bulb off } $0A \leq I \leq 2A$.
bulb dim }
bulb bright }

Concept of External resistor (R), internal resistance (r), Voltage (V), Potential drop (v) and Electromotive force (E):-

• External Resistor (R) refers to any component / appliance connected in the circuit


• Internal resistance (r) refers to the resistance offered by the chemicals inside the battery to the flow of current

Previous Papers vs Recent Papers

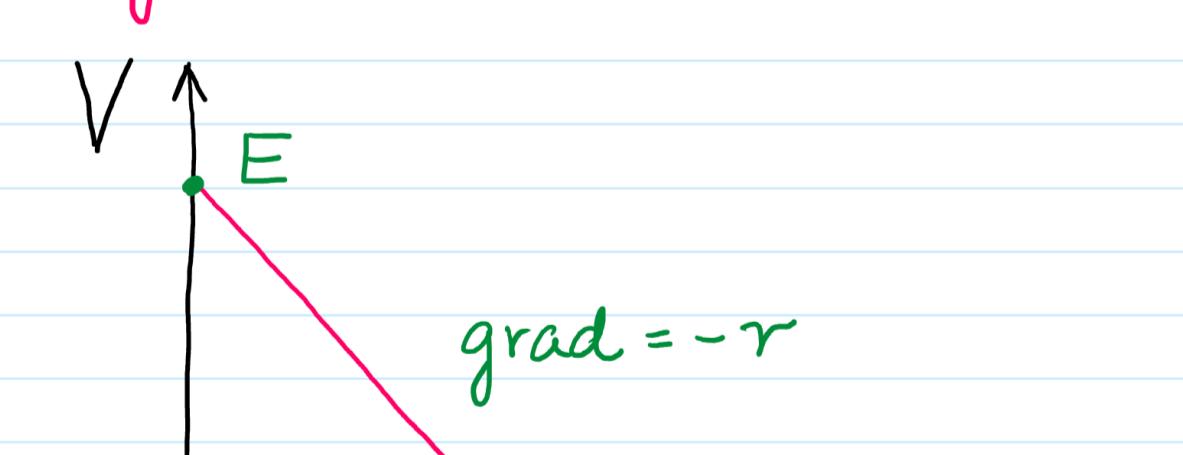

Cal. Current Supplied $I = \frac{6}{1+2} = 2A$

$$I = 2A$$

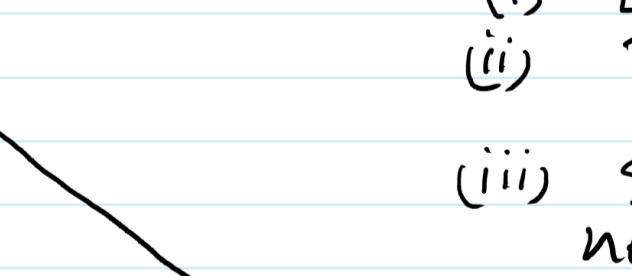

A straight Line graph with a negative gradient & a positive y-intercept

$V = Ir$

$V = IR$