

(i) Cal. length of AC required to achieve balance point?

Unitary method

General formula

$$180\text{cm} \rightarrow 6\text{V}$$

$$l \rightarrow 2\text{V}$$


$$V = \frac{l_{AC}}{l_{AB}} \times V_{P.C}$$

$$l(AC) = 60\text{cm}$$

$$2 = \frac{l_{AC}}{180} \times 6$$

$$l_{AC} = 60\text{cm}$$

Part (ii)

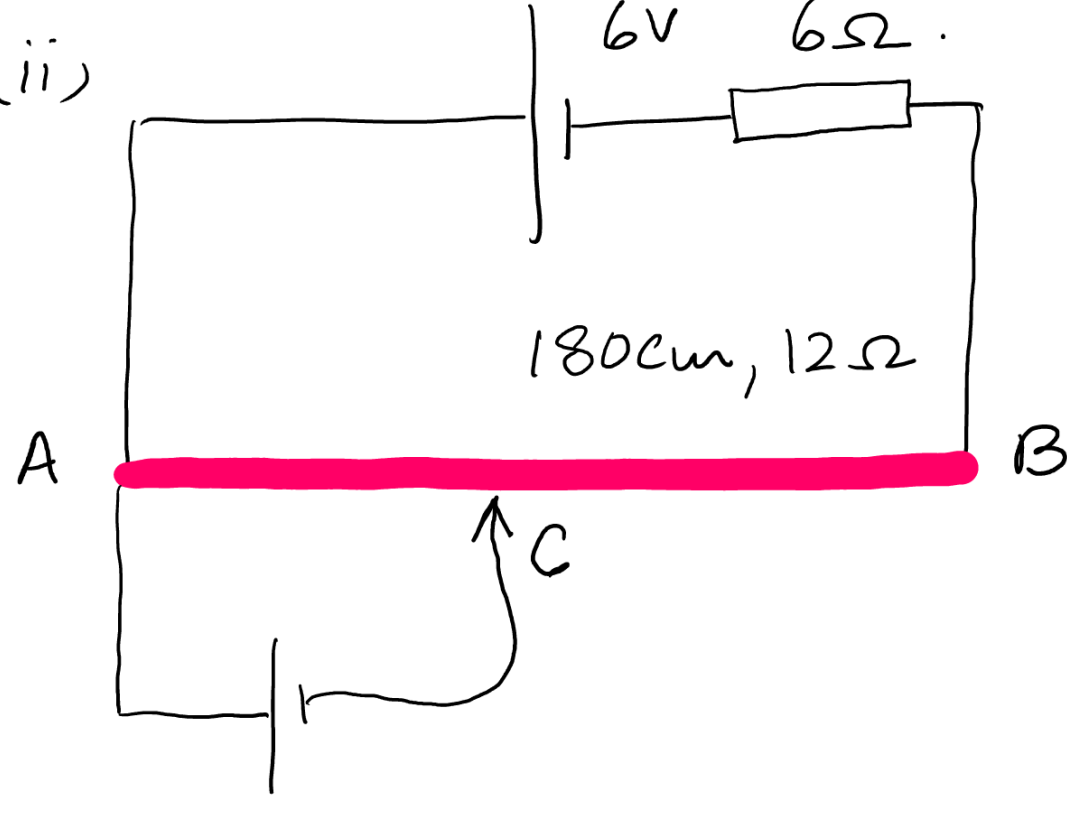

Cal. the new length of AC now required if an additional 6Ω resistor is placed with the Primary cell.

Step ① Find the voltage now available for the length AB using ratio method

$$\frac{12}{12+6} \times 6 = 4\text{V}$$

$$180\text{cm} \rightarrow 4\text{V}$$

$$l \rightarrow 2\text{V}$$


$$l = 90\text{cm}$$

Conclusion :: If an extra Resistor is placed in the Primary circuit as shown, it causes the length of balance point to **increase**.

Q Give an explanation as to why the length of the balance pt has increased i.e from (60cm → 90cm)

Ans :: If an additional Resistor is placed in the P. Circuit, the voltage **NOW AVAILABLE** for the Resistance wire (AB) reduces :: for the same voltage of Secondary cell a much longer length is now required to achieve a balance pt.

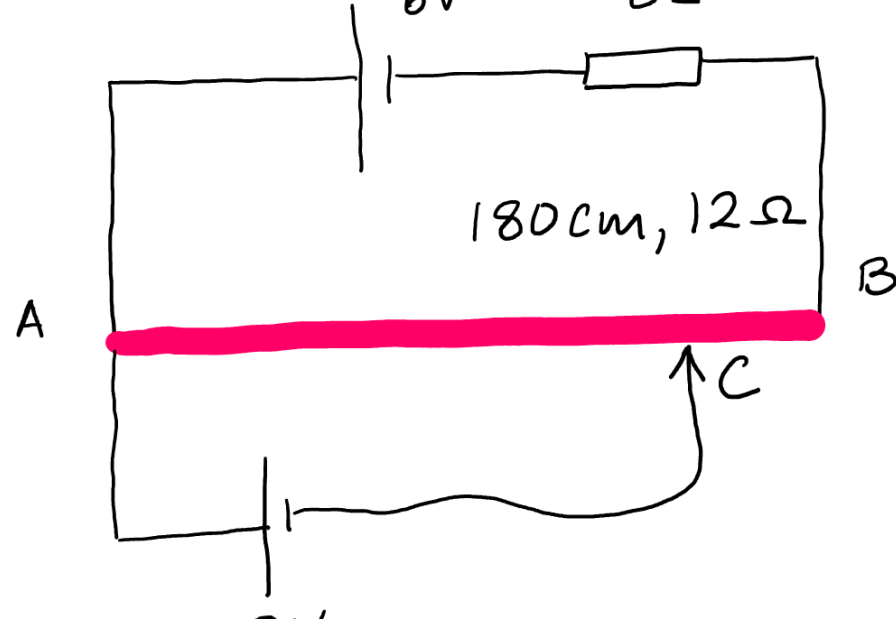Q :: What happens if 6Ω resistor is replaced by an 8Ω Resistor?



Step ① Cal Voltage across wire AB


$$V_{AB} = \frac{12}{12+8} \times 6 = 3.6\text{V}$$

$$\text{Step ② } 180\text{cm} \rightarrow 3.6\text{V}$$

$$l \rightarrow 2\text{V}$$

$$l_{AC} = 100\text{cm}$$

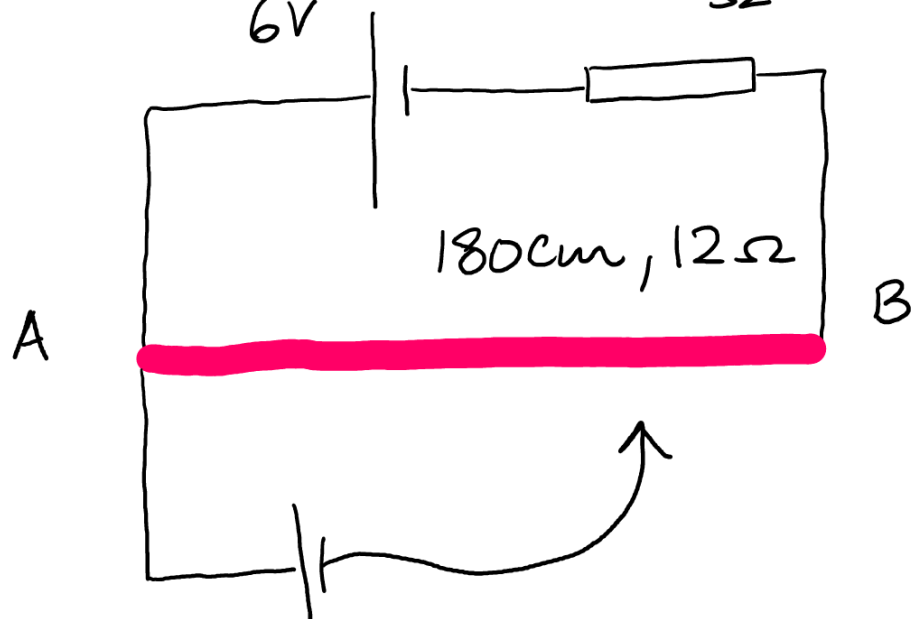Q :: What happens if 6Ω resistor gets replaced with a 30Ω resistor.



$$V(\text{wire}) = \frac{12}{12+30} \times 6$$


$$V_{\text{wire}} = 1.71\text{V}$$

No possibility of achieving Balancing point in this case

Conclusion :: Certain Rules must be kept in mind for a Potentiometer circuit to work properly

Rule ① +ve terminal of the P.C must be connected to the +ve terminal of the Secondary cell.

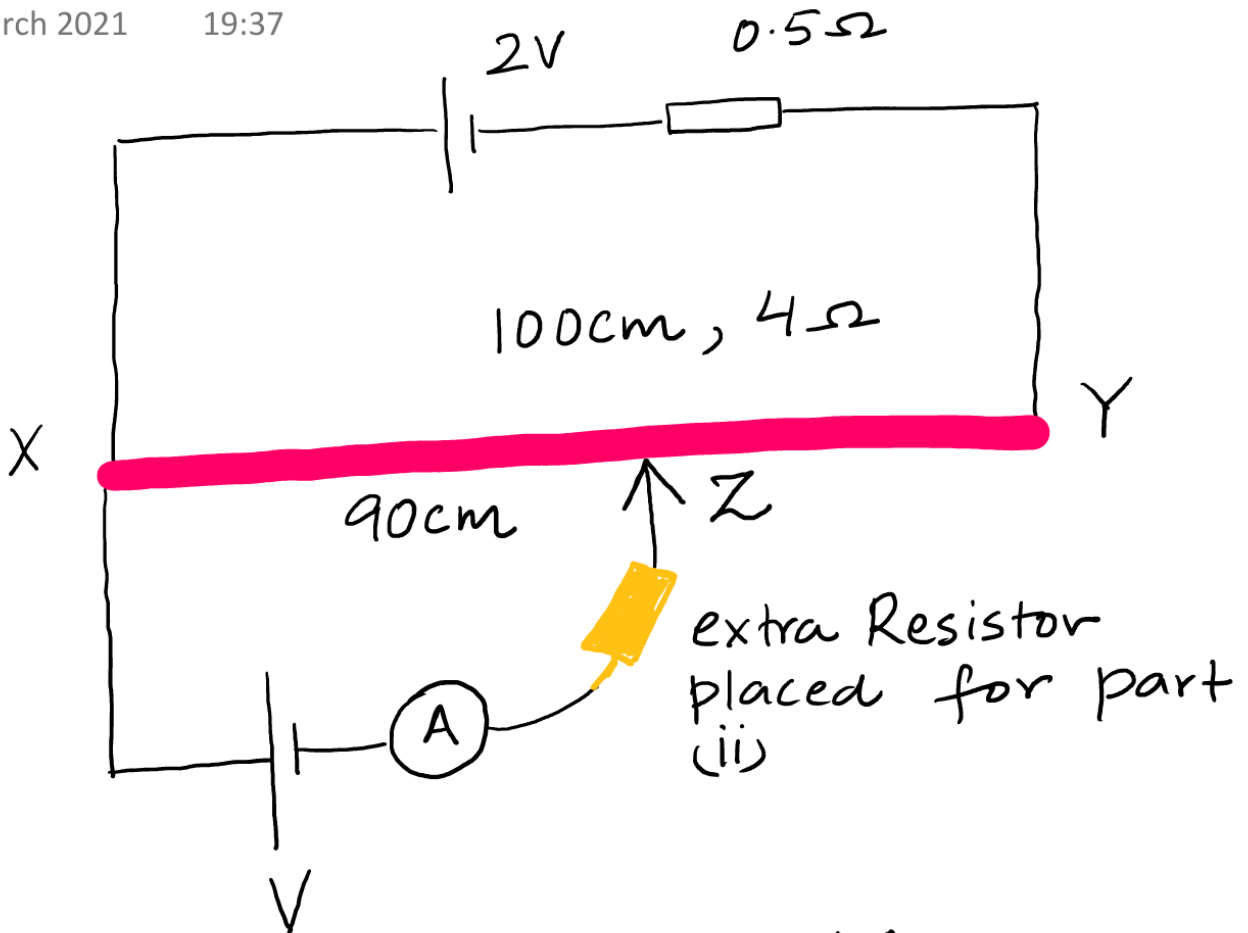Rule ② Voltage of the Secondary Cell must be less than or equal to the voltage available for the wire.



(i) If that (A) reads 0A (null deflection). Calculate the unknown voltage V?

Ans  $V_{(XY)} = \frac{4}{4+0.5} \times 2 = 1.78V$  step ①

Step ②  $100\text{cm} \rightarrow 1.78V$   
 $\therefore 90\text{cm} \rightarrow V$   
 $V = 1.6V$

(ii) Suggest why placing an extra resistor in the secondary circuit as shown will not have any effect on the balance pt.

Ans :: The term balance pt indicates that there is Zero Current in the Secondary circuit. Hence even if you place a resistor, based on  $V = IR$  the voltage across this resistor will be  $V = 0(R)$  i.e.  $0V$   $\therefore$  it will not consume / develop any voltage across itself hence its presence or absence does not affect the length of the balance point.