

DC Circuits

① KCL and KVL ✓

② Potentiometer (Today's class).

What is the purpose of a Potentiometer ::

A Potentiometer circuit is used to calculate voltage (unknown) of a Power supply.

How is the circuit constructed & how does it operate.

Working (next slide).