



[www.megalecture.com](http://www.megalecture.com) · [www.youtube.com/@megalecture](https://www.youtube.com/@megalecture)

Online tutoring for Cambridge IGCSE, O Level & A Level Physics

IGCSE PHYSICS 0625 · TOPICAL PAST PAPERS

# Uses of an Oscilloscope — Paper 1

Worked Answer Key (Multiple Choice)

**Fahad H. Ahmad**

Contact: **+92 323 509 4443**

M.Eng NUS Singapore · B.Eng NUST · 15+ years of teaching experience  
in Singapore, UAE & Pakistan · 60,000+ subscribers and 20 million+  
video lecture views.

[www.Megalecture.com](http://www.Megalecture.com) · +92 323 509 4443

# Uses of an Oscilloscope — Paper 1 · Worked Answer Key

These are **Megalecture worked answers** for the topical multiple-choice compilation on **Uses of an Oscilloscope (IGCSE Physics 0625, Paper 1)**. Every answer below was solved from first principles by the Megalecture team. Oscilloscope items use *time read from the time-base* (time = divisions × time-base setting), *voltage read from the Y-gain* ( $V = \text{divisions} \times Y\text{-gain setting}$ ) and *frequency*  $f = 1/T$ ; the speed of sound is taken as stated in each question. Use this key to mark your work and to see the one-line reasoning behind each correct letter. The compilation is organised into two parts, matching the original file — keep your eye on the part heading, as the exam-paper question numbering restarts in each part.

## Part A · Thermionic Emission, Cathode-Rays & Uses of an Oscilloscope

| Q # | Exam reference | Answer | Brief working / reason                                                                                                                                                                                                                                 |
|-----|----------------|--------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| A1  | M/J 16 P12     | C      | The hot filament emits <b>electrons</b> (negative), so the attracting plate must be <b>positive</b> . Thermionic emission needs a <b>high</b> filament temperature → positive plate, high temperature.                                                 |
| A2  | M/J 18 P11     | B      | Sound and echo peaks are <b>8 divisions</b> apart; each division = 0.01 s, so the round-trip time = $8 \times 0.01 = 0.08$ s. Distance to wall = $v t / 2 = 300 \times 0.08 / 2 = \mathbf{12\ m}$ .                                                    |
| A3  | M/J 18 P12     | C      | With the time-base on, a d.c. input gives a <b>horizontal line</b> . Deflection = $V / Y\text{-gain} = 1.5 / 0.5 = \mathbf{3\ divisions}$ , so the line sits 3 divisions above the centre → trace <b>C</b> .                                           |
| A4  | O/N 16 P11     | A      | The bright spot is moved by the electric field between the deflecting plates P and Q. To shift the spot you must <b>apply a voltage (p.d.) between plates P and Q</b> .                                                                                |
| A5  | O/N 17 P11     | B      | A hot metal filament releases <b>electrons</b> by thermionic emission.                                                                                                                                                                                 |
| A6  | O/N 18 P11     | A      | The trace covers 8.0 cm in 24 ms, so $1.0\ \text{cm} \equiv 3.0\ \text{ms}$ . The peaks are 3.0 cm apart = 9.0 ms for the round trip; time to reach the wall = half of this = <b>4.5 ms</b> .                                                          |
| A7  | O/N 18 P12     | C      | With a d.c. input and the <b>time-base off</b> , the spot is deflected only vertically (no horizontal sweep), giving a <b>vertical line</b> → trace <b>C</b> .                                                                                         |
| A8  | O/N 19 P11     | C      | A continuous electron flow needs a <b>hot filament</b> (1) to release electrons and a <b>high positive potential</b> (3) to pull them away. A gas or magnetic field is not required → <b>1 and 3</b> .                                                 |
| A9  | O/N 19 P11     | C      | Pulse height = 2 cm (the "1 cm" marker is one square), so $v = Y\text{-gain} \times \text{height} = 2 \times 2 = \mathbf{4\ V}$ . One full cycle (on + off) = 2 cm, so $T = 2 \times 0.01 = 0.02$ s and $f = 1/T = \mathbf{50}$ → $v = 4$ , $f = 50$ . |

| Q # | Exam reference | Answer | Brief working / reason                                                                                                                                                                                                         |
|-----|----------------|--------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| A10 | O/N 20 P12     | A      | The trace is a sine wave swinging both sides of the centre line, so the signal is <b>a.c.</b> Amplitude (peak deflection) = 1.5 divisions, so amplitude = $1.5 \times 2 = 3 \text{ V} \rightarrow \text{a.c., } 3 \text{ V}$ . |

## Part B · Action and Use of Circuit Components

| Q # | Exam reference | Answer | Brief working / reason                                                                                                                                                                                                                                                                                               |
|-----|----------------|--------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| B1  | M/J 16 P11     | A      | The component that conducts in one direction only is the <b>diode</b> (triangle + bar) $\rightarrow$ symbol <b>A</b> . (B is a lamp, C is a fuse, D is a different component.)                                                                                                                                       |
| B2  | M/J 16 P11     | B      | V across the LDR = $6.0 \times R_{\text{LDR}} / (R_{\text{th}} + R_{\text{LDR}})$ . This is smallest when $R_{\text{LDR}}$ is small (bright/light: $500 \Omega$ ) and $R_{\text{th}}$ is large ( <b>cold</b> : high $\Omega$ ) $\rightarrow$ <b>cold and light</b> .                                                 |
| B3  | M/J 16 P12     | B      | Series divider: $V_1$ across the fixed $6.0 \Omega$ , $V_2$ across R. Raising R increases its share of $6.0 \text{ V}$ , so <b><math>V_1</math> decreases and <math>V_2</math> increases</b> .                                                                                                                       |
| B4  | M/J 17 P11     | C      | $V_{\text{LDR}} = 2.0 \text{ V}$ means $R_{\text{LDR}}$ is one third of the total, i.e. $R_{\text{th}} = 2 R_{\text{LDR}}$ . This fits warm room ( $R_{\text{th}} = 1000 \Omega$ ) with bright light ( $R_{\text{LDR}} = 500 \Omega$ ): $V = 6 \times 500/1500 = 2.0 \text{ V} \rightarrow$ warm room, bright light. |
| B5  | M/J 18 P11     | A      | Largest current needs the smallest total resistance, so both components must have low resistance: thermistor <b>hot</b> (high temperature) and LDR in <b>bright light</b> $\rightarrow$ high temperature, in bright light.                                                                                           |
| B6  | M/J 18 P11     | B      | R is in parallel with the lower resistor. Increasing R raises the lower combined resistance, so it takes a larger share of the supply: <b><math>V_1</math> (upper) decreases and <math>V_2</math> (lower) increases</b> .                                                                                            |
| B7  | M/J 18 P12     | D      | An LDR is drawn as a resistor (rectangle) with two arrows pointing <b>in</b> towards it (light falling on it) $\rightarrow$ symbol <b>D</b> . (A is an LED; B is a thermistor; C is a variable resistor.)                                                                                                            |
| B8  | M/J 19 P11     | D      | The starter-motor circuit carries a very large current ( $100 \text{ A}$ ), so it needs short, thick (low-resistance) wires; the ignition-switch circuit carries only $1 \text{ A} \rightarrow$ <b>the ignition switch circuit carries a smaller current than the starter motor circuit</b> .                        |
| B9  | M/J 19 P11     | A      | To recharge, current must flow <b>into</b> the battery's + terminal. Only a single series diode pointing towards + (as in <b>A</b> ) lets current flow that way during the correct half-cycle; B drives current the wrong way, and C/D place the diode in parallel.                                                  |
| B10 | O/N 16 P11     | D      | Bands yellow–violet–orange = 4, 7, then $\times 10^3$ : $R = 47 \times 1000 = 47\,000 \Omega$ .                                                                                                                                                                                                                      |
|     | O/N 16 P12     |        |                                                                                                                                                                                                                                                                                                                      |

| Q #        | Exam reference | Answer   | Brief working / reason                                                                                                                                                                                                                               |
|------------|----------------|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <b>B11</b> |                | <b>C</b> | As temperature falls, the thermistor's resistance <b>increases</b> . It then takes a larger share of the supply, so the p.d. across the fixed resistor (the voltmeter reading) <b>decreases</b> → resistance increases, voltmeter reading decreases. |
| <b>B12</b> | O/N 17 P11     | <b>B</b> | An LED conducts (and lights) only when forward biased — current in one direction. The triangle points to the right, so it emits light only when the current is <b>towards the right only</b> .                                                       |
| <b>B13</b> | O/N 17 P12     | <b>A</b> | A thermistor's resistance rises when it gets colder (decrease in temperature); an LDR's resistance rises when it gets darker (decrease in brightness) → <b>decrease in temperature and decrease in brightness</b> .                                  |
| <b>B14</b> | O/N 18 P12     | <b>D</b> | Least resistance needs both components at low resistance: thermistor <b>hot</b> (low R) and LDR in <b>light</b> (low R) → <b>hot and light</b> .                                                                                                     |
| <b>B15</b> | O/N 19 P11     | <b>A</b> | A diode in series gives <b>half-wave rectification</b> : only one polarity passes, the blocked half is flat at the zero line. The trace is positive humps separated by flat sections → trace <b>A</b> .                                              |
| <b>B16</b> | O/N 20 P11     | <b>C</b> | (Same set-up as B4.) $V_{LDR} = 2.0 \text{ V}$ needs $R_{th} = 2 R_{LDR}$ : warm room ( $1000 \Omega$ ) with bright light ( $500 \Omega$ ) gives $6 \times 500/1500 = \mathbf{2.0 \text{ V}}$ → warm room, bright light.                             |
| <b>B17</b> | O/N 20 P12     | <b>C</b> | Equal X and Y give output = 6 V across Y. Halving X makes output = $12 \times Y/(\frac{1}{2}X + Y) = 12 \times 1/1.5 = 8 \text{ V}$ . Change = $8 - 6 = \mathbf{+2.0 \text{ V}}$ .                                                                   |

**Note from Megalecture.** This compilation combines two syllabus areas that share the same file ("thermionic emission / cathode-rays / oscilloscope" and "action and use of circuit components"); the exam-paper question numbers restart in each part, so we have labelled them A1–A10 and B1–B17. Items B4 and B16 are the same potential-divider question repeated, and are answered consistently above. These are original Megalecture worked solutions prepared for revision use.